

VLSI LAB REPORT

MID SEMESTER

Submitted by

A.Anand Menon (08EC01)

Dilip Kushwaha(08EC21)



Experiment 1:



Study the V-I characteristics of NMOS Transistor

Objective:

Study the input and output characteristics of NMOS Transistor, effects of L , W , V_{TO} , λ , V_{SB} and temperature on the behavior of the transistor.

DC Sweep

I_d vs V_{gs}

  


I_d vs V_{ds}

With increase in the values of V_{dd} and V_{gs} , the drain current increases.


Variation with Lambda

LAMBDA = 0.1

 

I_d vs V_{gs}

 
Value of current for $V_{gs}=10V$
at $V_{dd}=8V$ is 6



I_d vs V_{ds}


Variation with Lambda

LAMBDA = 0.3

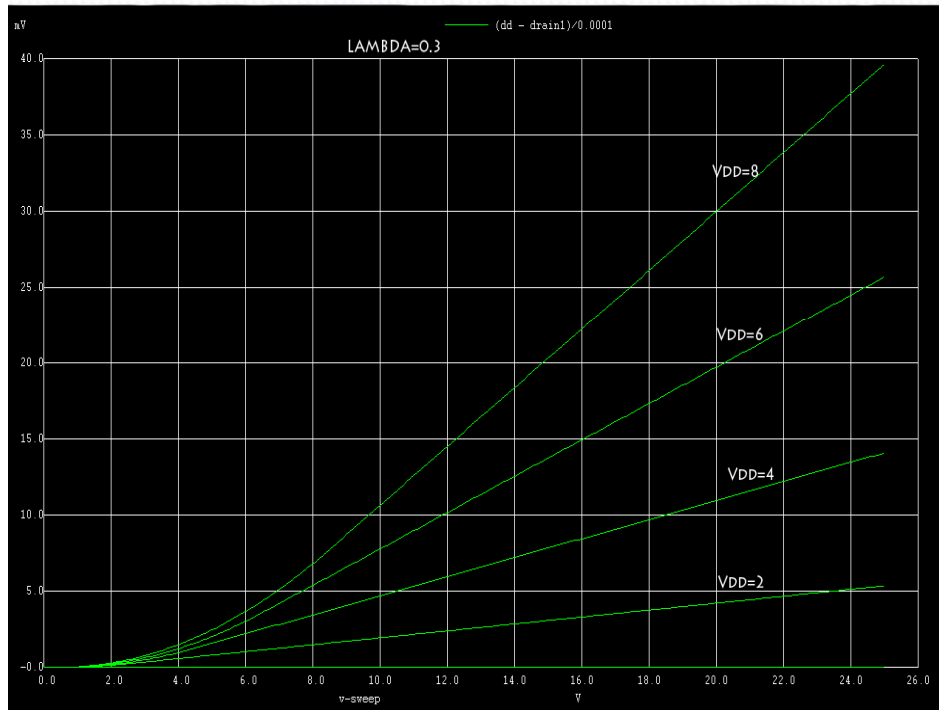

I_d vs V_{gs}

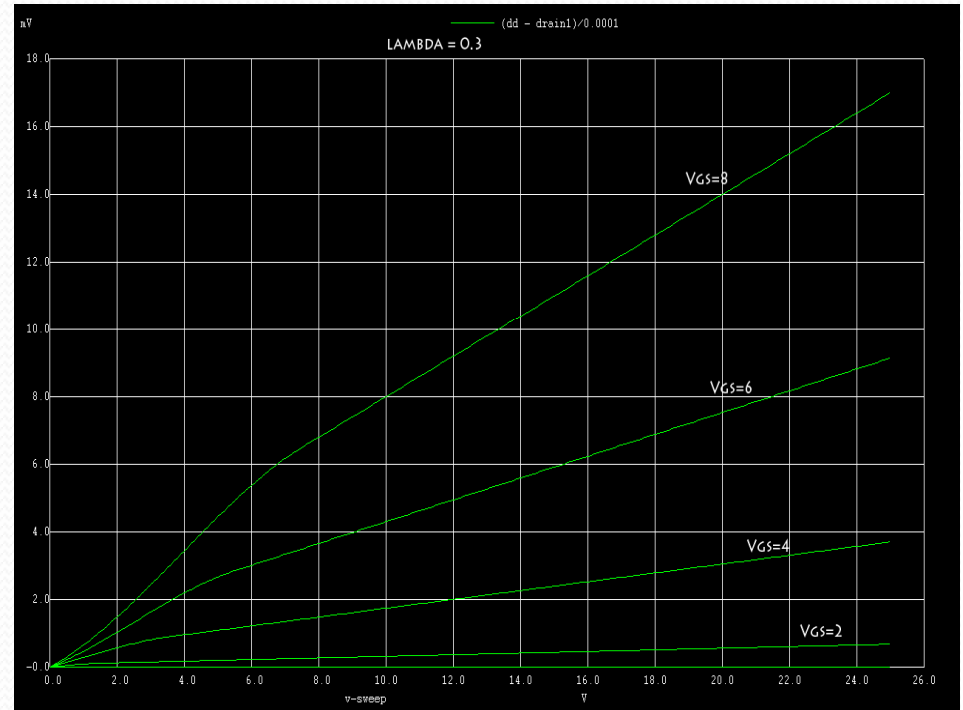
Value of current for $V_{gs}=10V$
at $V_{dd}=8V$ is 11



I_d vs V_{ds}


Variation with Lambda

LAMBDA = 0.5

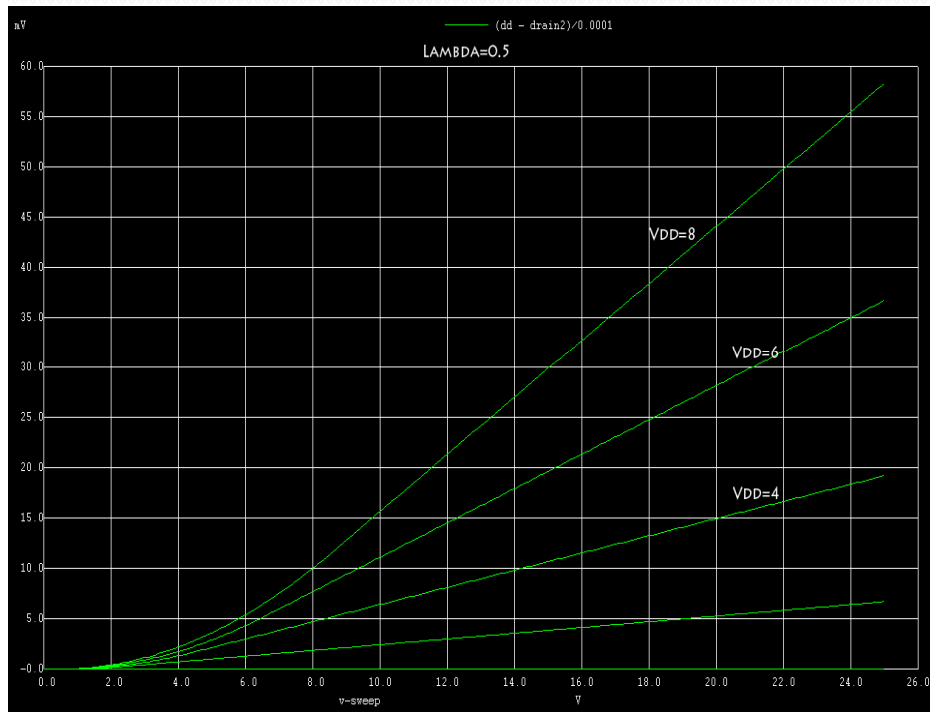

I_d vs V_{gs}

 Value of current for $V_{gs}=10V$
at $V_{dd}=8V$ is 15



I_d vs V_{ds}




Variation with Lambda

Conclusion :

As the value of Lambda increases, the current also increases. This holds true for both Vdd sweep as well as Vgg sweep.


Hence, current is directly proportional to Lambda.

Variation with Temperature

 


I_d vs V_{gs}

TEMP = 0

 


I_d vs V_{ds}

Variation with Temperature

 


I_d vs V_{gs}

TEMP = 25

 


I_d vs V_{ds}

Variation with Temperature

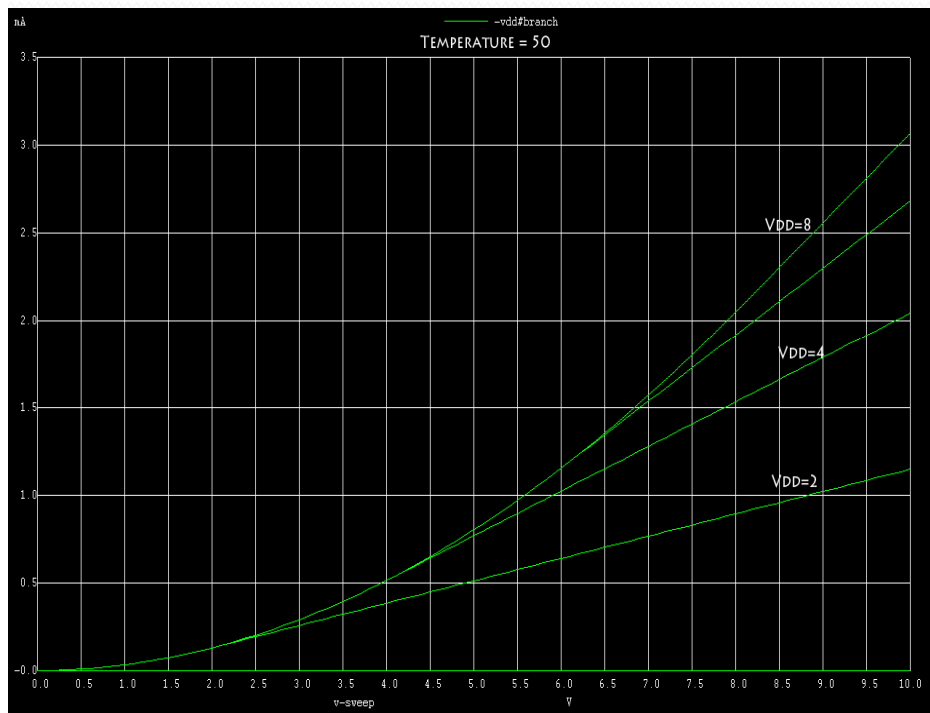

I_d vs V_{gs}

TEMP = 50

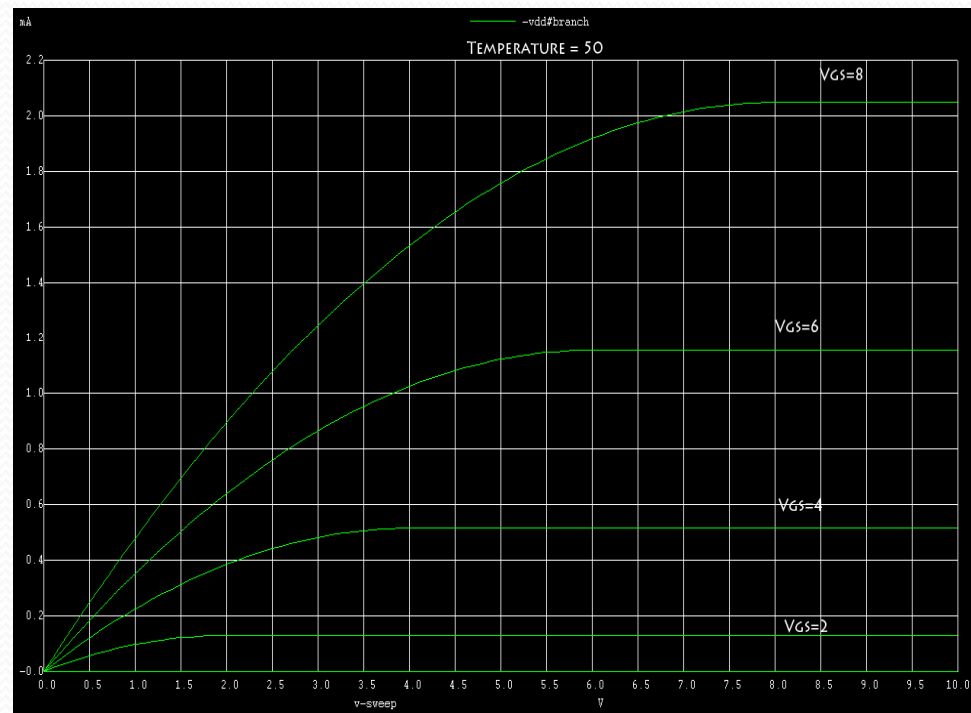

I_d vs V_{ds}




Variation with Temperature

Conclusion :


As the value of temperature increases, the current decreases. This holds true for both Vdd sweep as well as Vgg sweep.

Hence, the current is inversely proportional to the temperature.

Variation with V_{sb}

 


$V_{sb} = 0.2$ V

 

$V_{sb} = 0.4$ V

Variation with V_{sb}

 


$$V_{sb} = 0.6 \text{ V}$$

Conclusion :


As the value of V_{sb} increases, the current decreases. This holds true for both V_{dd} sweep as well as V_{gg} sweep.

Hence, the current is inversely proportional to V_{sb} .

Variation with V_{T0}

 

I_d vs V_{ds}

 

I_d vs V_{gs}




Variation with V_{T0}

Conclusion :

As the value of V_{T0} increases, the current decreases. This holds true for both V_{dd} sweep as well as V_{gg} sweep.

Hence, the current is inversely proportional to V_{T0} .

Variation with length

 


Conclusion :

As the value of length increases, the current decreases. This holds true for both V_{dd} sweep as well as V_{gg} sweep.

Hence, the current is inversely proportional to length.

Variation with width

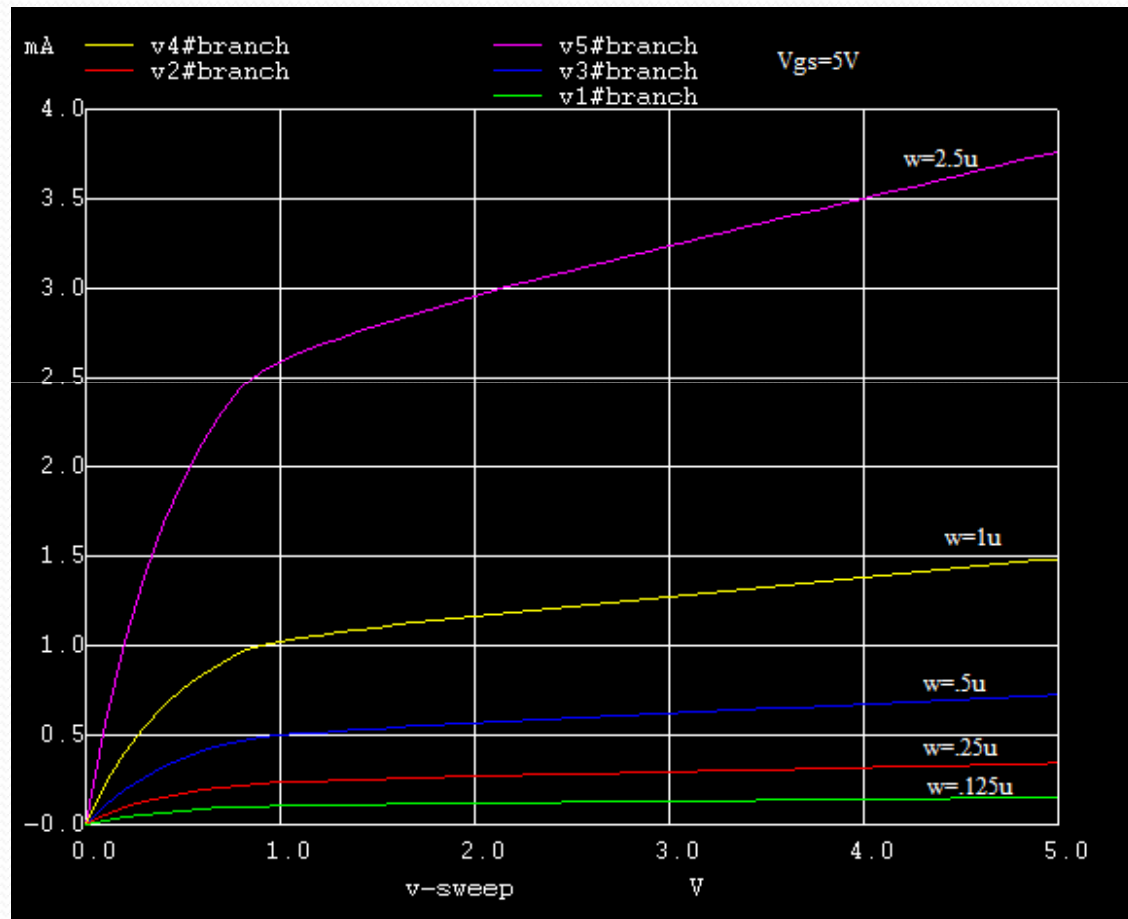

Conclusion :

As the value of width increases, the current increases. This holds true for both V_{dd} sweep as well as V_{gg} sweep.

Hence, the current is directly proportional to width.



Experiment 2:

Study of MOS inverter with passive resistive load


Objective:

Study the transfer function, Noise margin, effect on rise time, fall time, propagation delay, power and energy consumed of a MOS Inverter for various L , W of the transistor, load capacitance and rise/fall time of input


Vout vs Vin for an NMOS with resistive load

```
*nmos inverter with passive resistive load
.include tsmc_o25_level3.model
*spice netlist
m1 drain vin 0 0 cmosn l=.25u w=.75u
*resistance
r1 drain vd 20k
*supply source
vdd vd 0 dc 5
vgg vin 0 dc 5
*responses
.dc vgg 0 5 0.1
*vgg pulse (0 5 0 0.1ns 0.1ns 50ns 100ns)

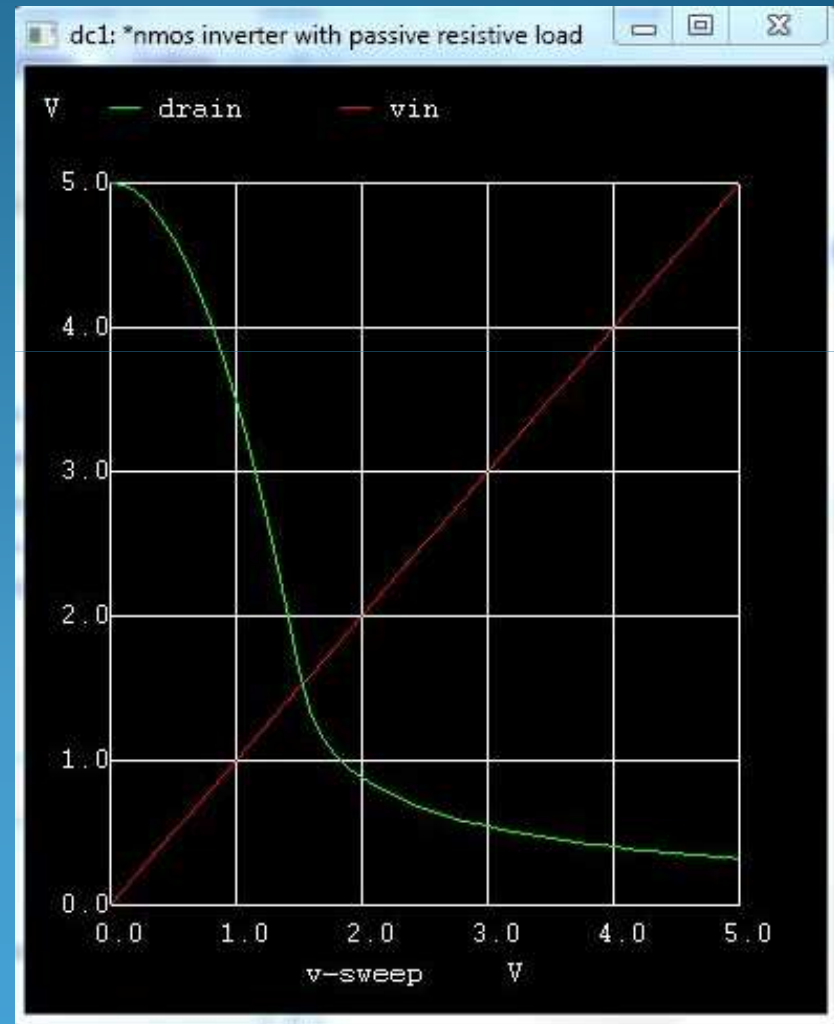.control
run
Setplot dc1
Plot drain vin
.endc
.end
```




 Transient response for inverter with variation in length




With decrease in length we have stronger ON

 Transient response for NMOS with varying length





□ Graph shows that V_{ih} increases with increase in width

 Transient response with varying resistance



- ❑ With increase in resistance Noise Margin Low also decreases
- ❑ But gain increases

  
Effect of change resistance on rise time and fall time




- ❑ Fall time decreases with increase in Resistance
- ❑ Rise time decreases with increase in Resistance

Effect of change in W/L ratio on rise time and fall time

1. Fall time

 


2. Rise time

 


Output capacitance

 
1. V_{out} across capacitance for square wave input



 2.Vout across capacitance for low to high input



3.Vout across capacitance for high to low input

 




Experiment 3:

Study of MOS Inverter with active load – NMOS and PMOS


Objective:

For a MOS Inverter with active load – NMOS and PMOS, study the Noise Margin, effect on rise time, fall time, propagation delay, power and energy consumed with variation in L and W.


Current Variation with NMOS Load

 


Transient Analysis with NMOS Load (Fall)

 


Transient Analysis with NMOS Load (Rise)

 


Transient Analysis with PMOS Load (Fall)

 


Transient Analysis with PMOS Load (Rise)

 

VTC for NMOS Load

 

VTC for PMOS Load

 




Experiment 4:

Study of CMOS Inverter


Objective:

Study the Transfer function, Noise Margin, effect on rise time, fall time, propagation delay, power and energy consumed of a CMOS inverter with variation in L and W.

Transfer Function


 


Variation in current with W/L

 




Rise time

  


Fall time

Variation in power with W/L

 

Power Dissipation for pulse input

 




Experiment 5:

Study of CMOS Gates


Objective:

Study the Behavior Transfer function, Noise Margin, effect on rise time, fall time, propagation delay, power and energy consumed of CMOS gates like NAND, NOR functions like AOI and XOR with variation in L and W.


NAND Output

 


NAND DC Analysis

 


NAND Propagation Delay

 


NOR Output

 

NOR DC Analysis

 

XOR Output

 

AOI Hazard

