

# VLSI DESIGN LAB

## MODULE 1 REPORT : CIRCUIT SIMULATION WITH NGSPICE

Submitted by :

Amol Kadam Maroti

08ec06


Ankit Anand

08ec10

## Lab 1:


Study the input and output characteristic of NMOS transistor.  
effect of length ,width , $V_{to}$  , $V_{sb}$  , $\lambda$  , and temperature on the behavior of transistor.

\* $I_d$  vs  $V_{dd}$ :

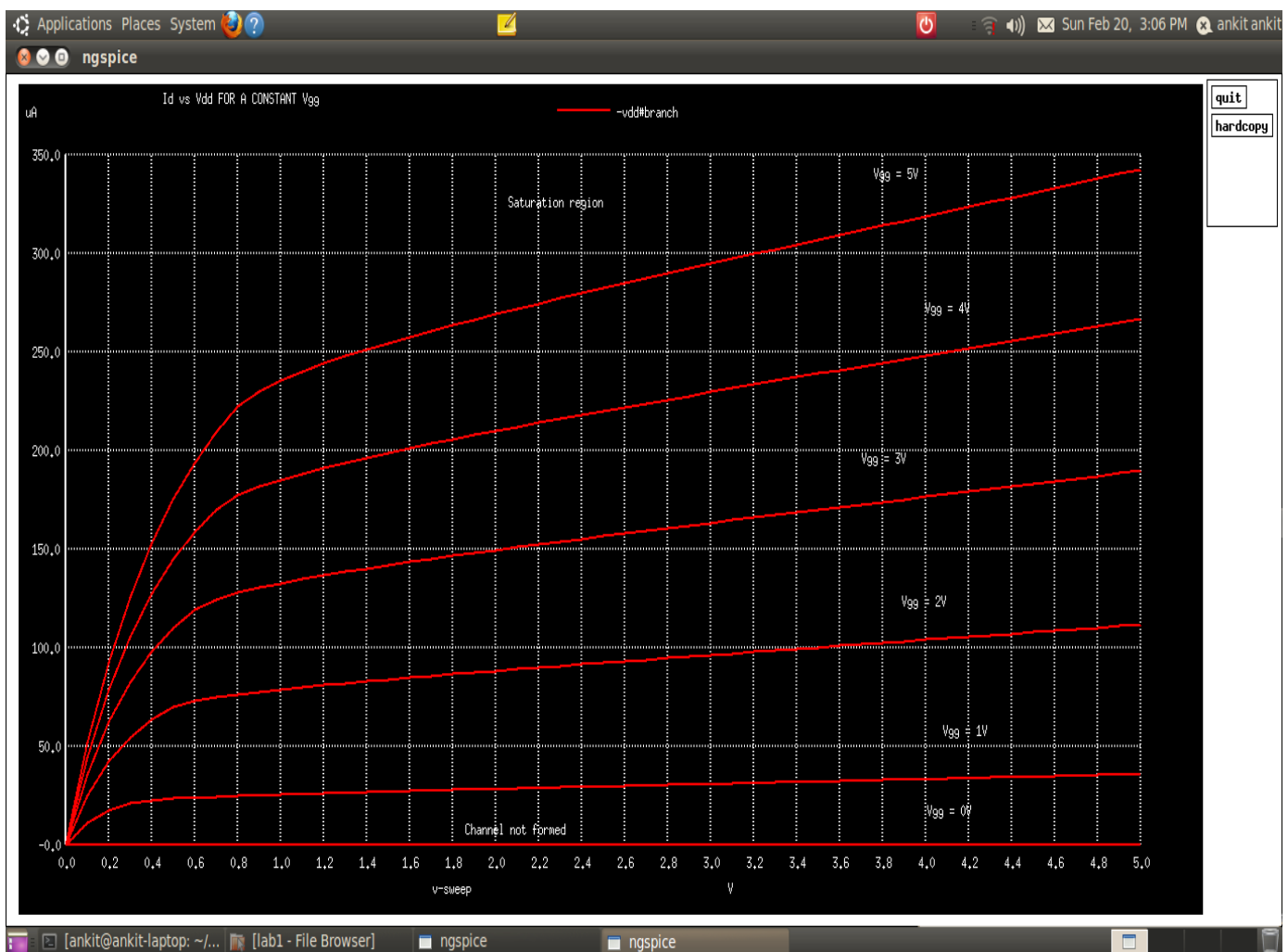

The  $I_d$  vs  $V_{dd}$  curve is at first linear then becomes varies slowly in saturation region due to channel length modulation which should be otherwise constant.

\*Id vs Vgg:

 

Initially the current is zero as the channel is not formed. This is till  $V_{gs}$  crosses the threshold voltage. Then the current varies almost linearly

## Lambda variation : Id vs Vdd




The current for different values of  $\lambda$ . The variation is due to the  $(1 + \lambda V_{DS})$  factor in the expression of the current.

## Lambda variation : $I_d$ vs $V_{gg}$



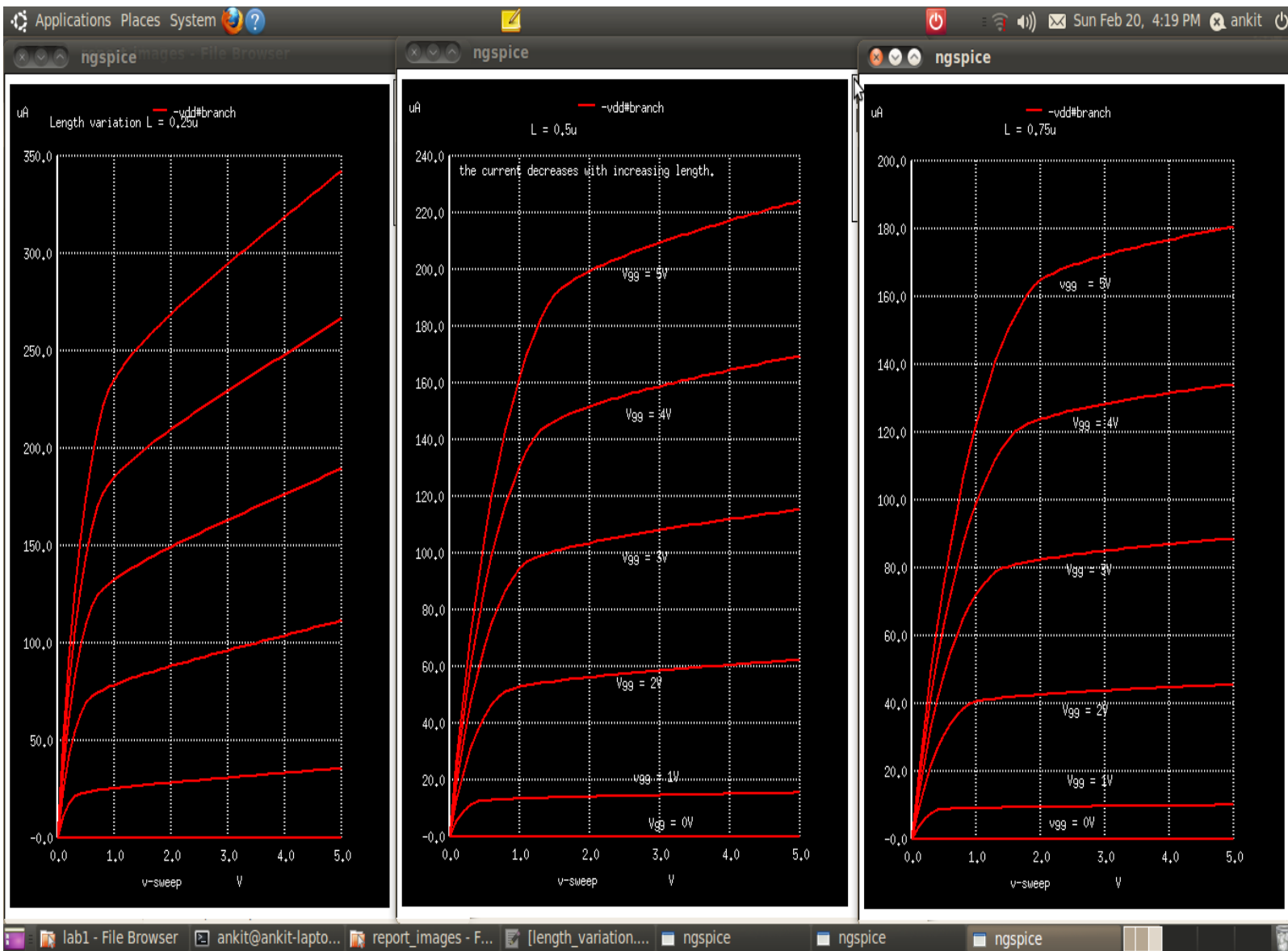
## Length variation : $I_d$ vs $V_{dd}$ :




When  $V_{gg}$  is more than  $V_{th}$ , the current varies as shown above with  $V_{dd}$ . If the length parameter is changed then the current decreases with increase in length which can be seen by the values on y-axis.

length variation :

 

The above curve shows the effect of length variation on current with respect of  $V_{gg}$  for a constant value of  $V_{dd}$ .


## Temperature variation :

 


The above curve shows the variation of current with Vgg and Vdd at temperature of 0.




## Temperature Variation: at temp = 25

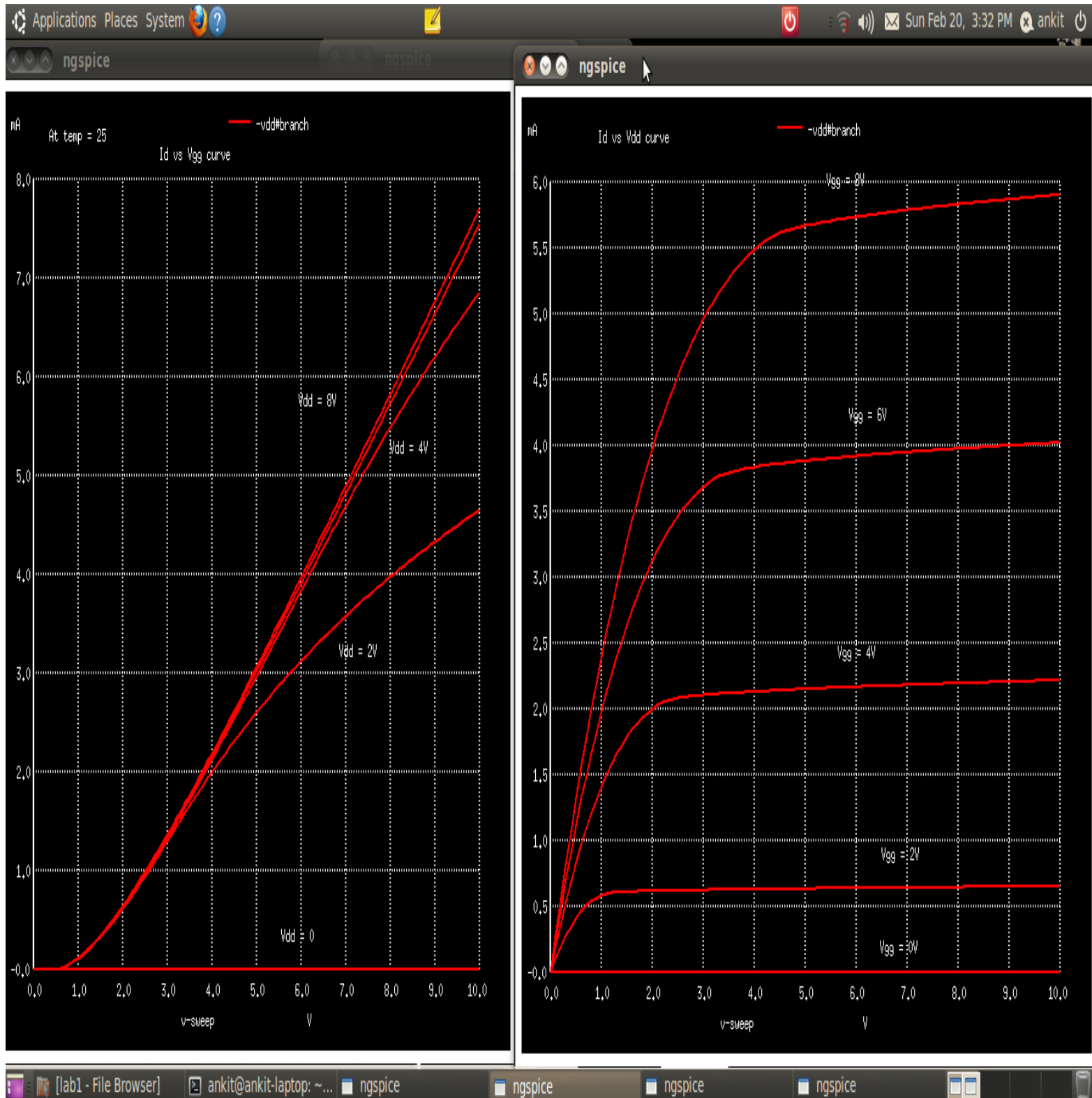

Temperature variation : at temp = 50

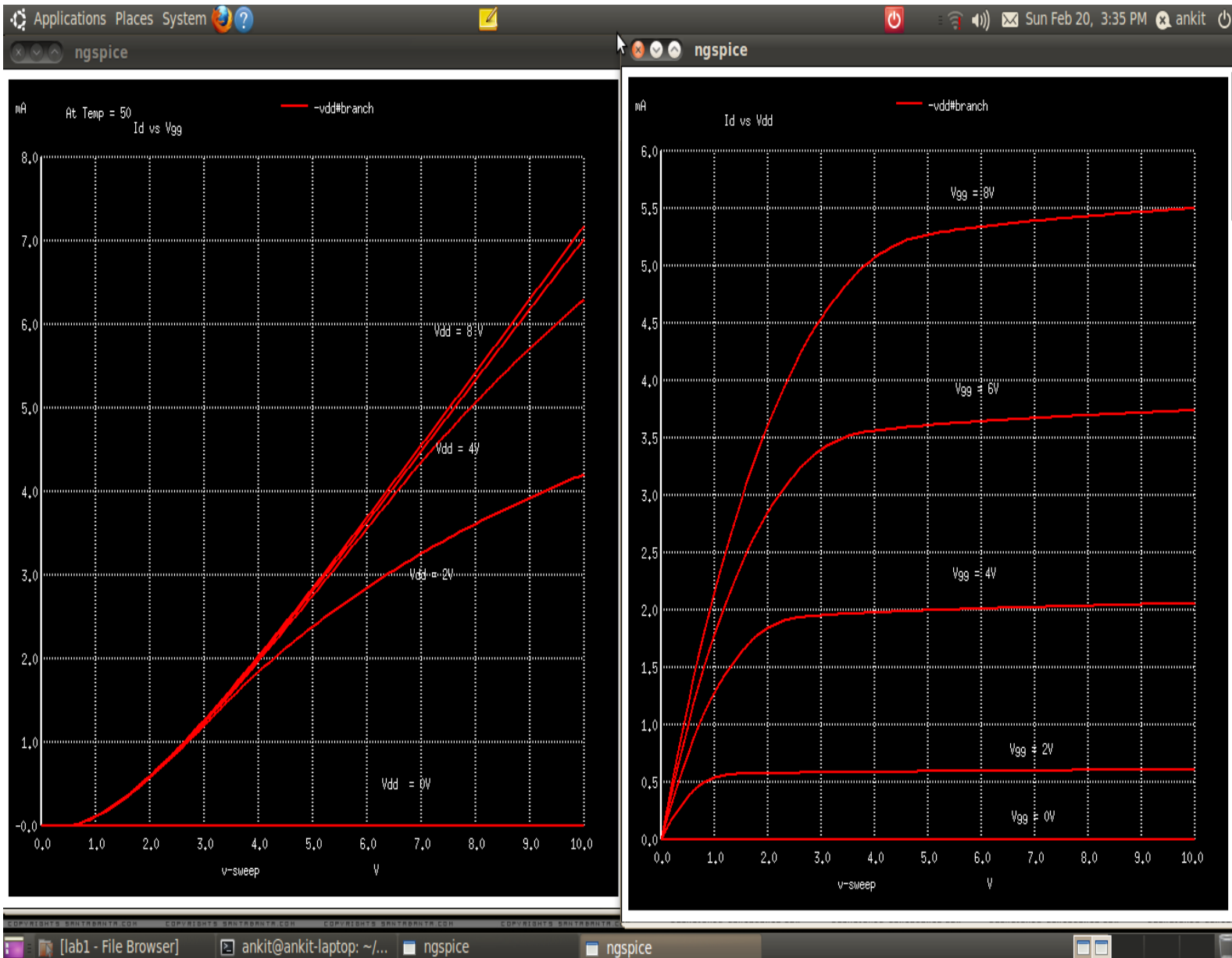


Vsb variation :

 

As  $V_{sb}$  increases the threshold voltage increases, so initially the current is zero till the gate voltage crosses the threshold voltage.

# Vsb variation

 

Vto variation :




Since the threshold voltage increases with the increases with the increase in the source to body voltage ,so the current also increases.

Vto variation :




## Width variation :

 


The current increases linearly with the increase in the width parameter.

## Width variation :

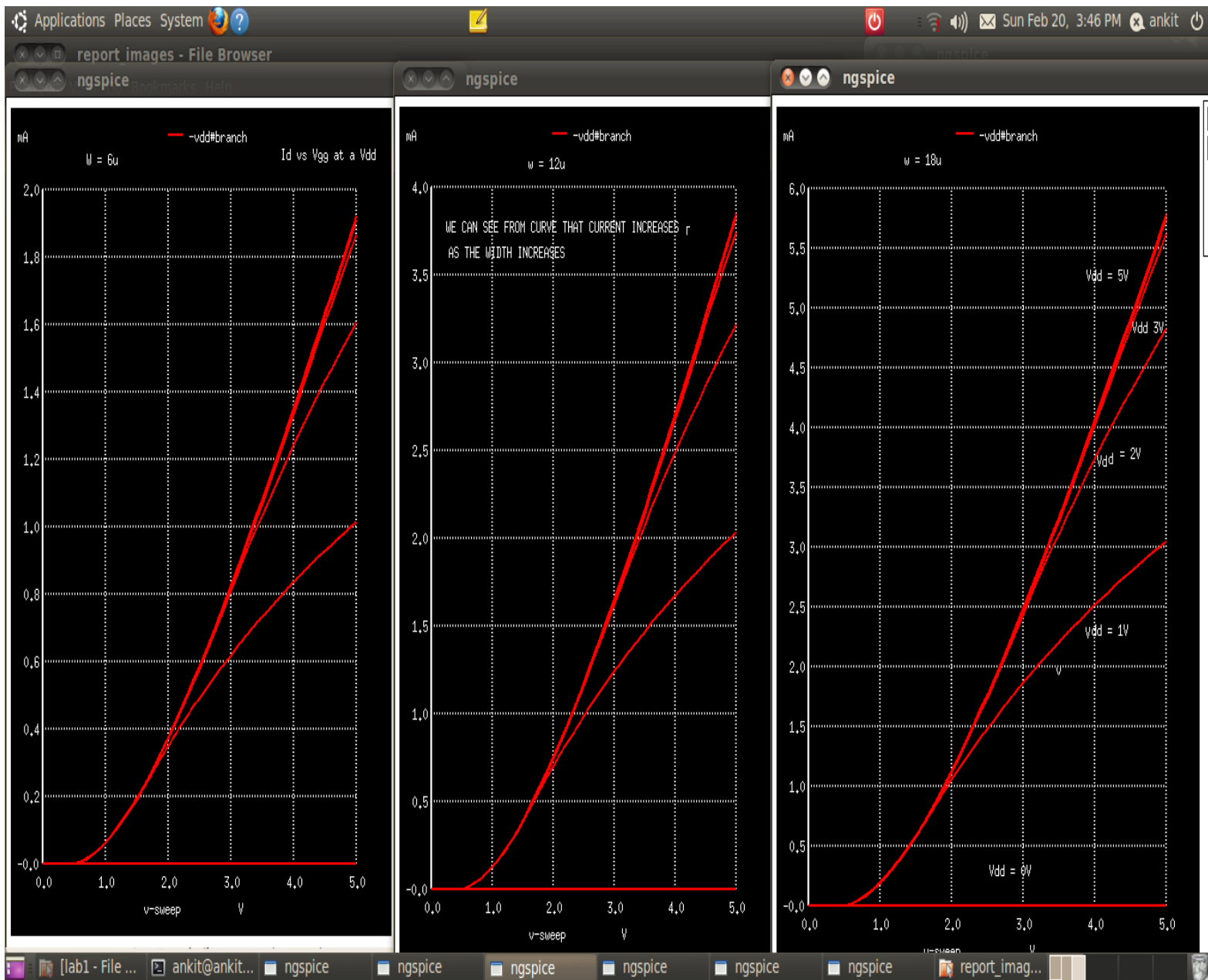




## Resistive load inverter:

 


As usual the current decreases with the increase in resistance.


## W/L variation

 

 
The effect of variation in the the current with respect to  $w/l$  is shown above. The current increases with the increase in the  $w/l$ .




Nmos load :

 


VTC of Inverter:

 


Pmos\_load\_tf

 

Pmosload\_cap

 


Nmos\_load\_tf:

 





Nmos load with Various w/l:

 


Pmos\_load :

 


Pmos load with capacitance:

 

Cmosp\_dc :

 


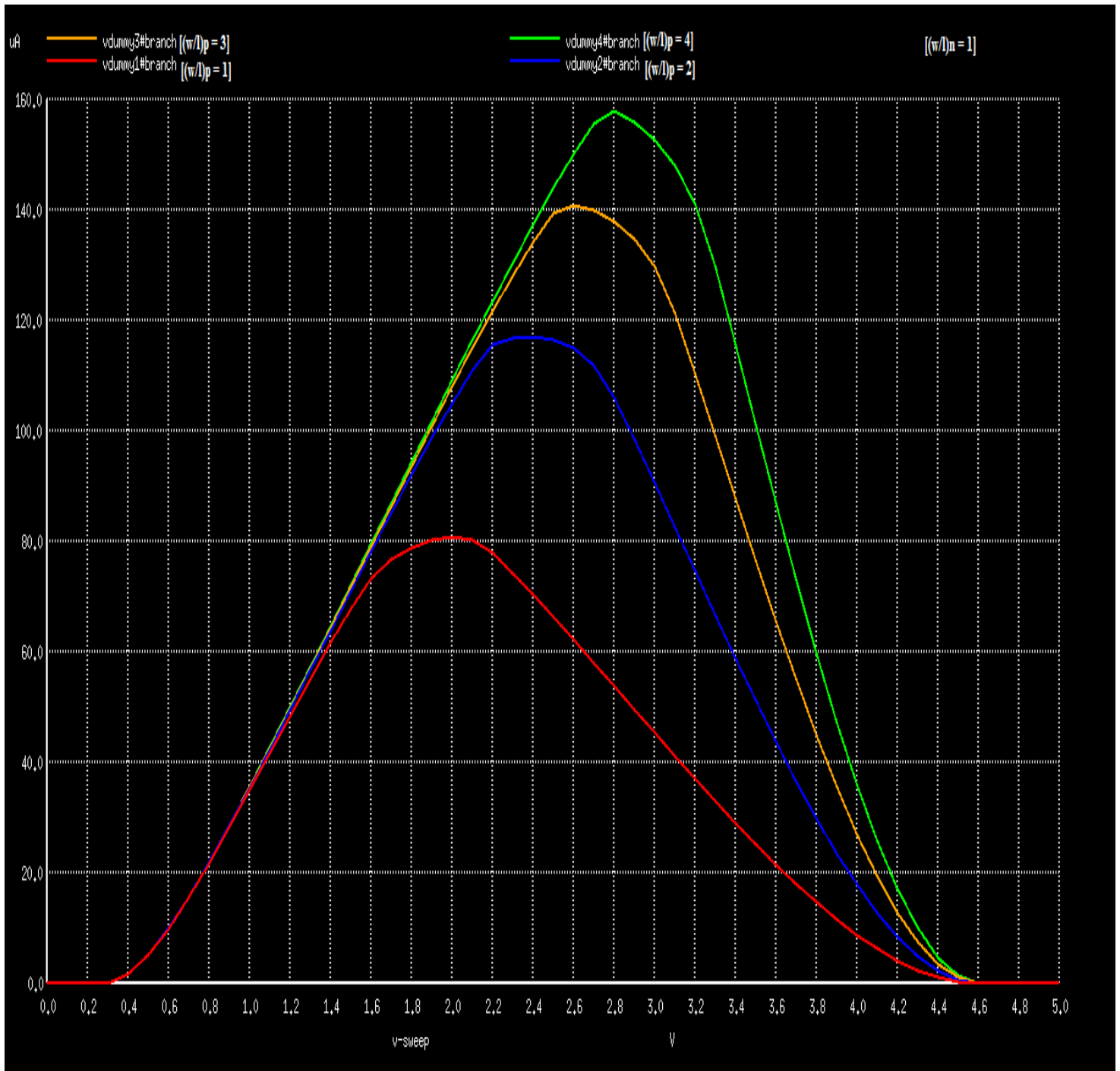The variation in power with different values of  $w/l$ :




Since the current increases with increase in  $w/l$ ...so the power also increases.

 
Transient analysis with various w/l values:



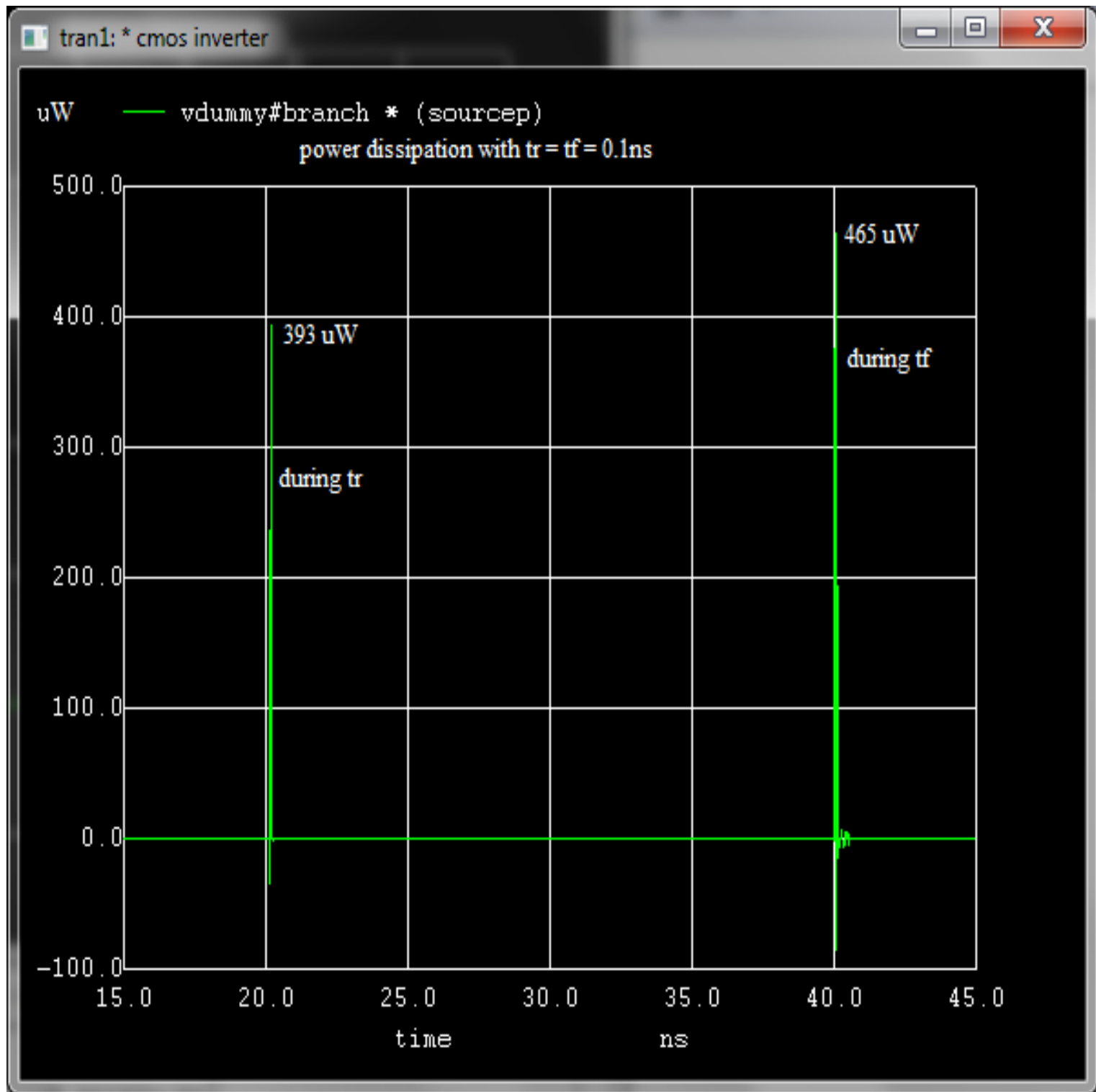Power dissipation during rise time and fall time:




 Power dissipation for  $t_r = t_f = 0.5\text{ns}$ :






 
Cmos inverter with various values of output capacitance:




Rise time with loads :

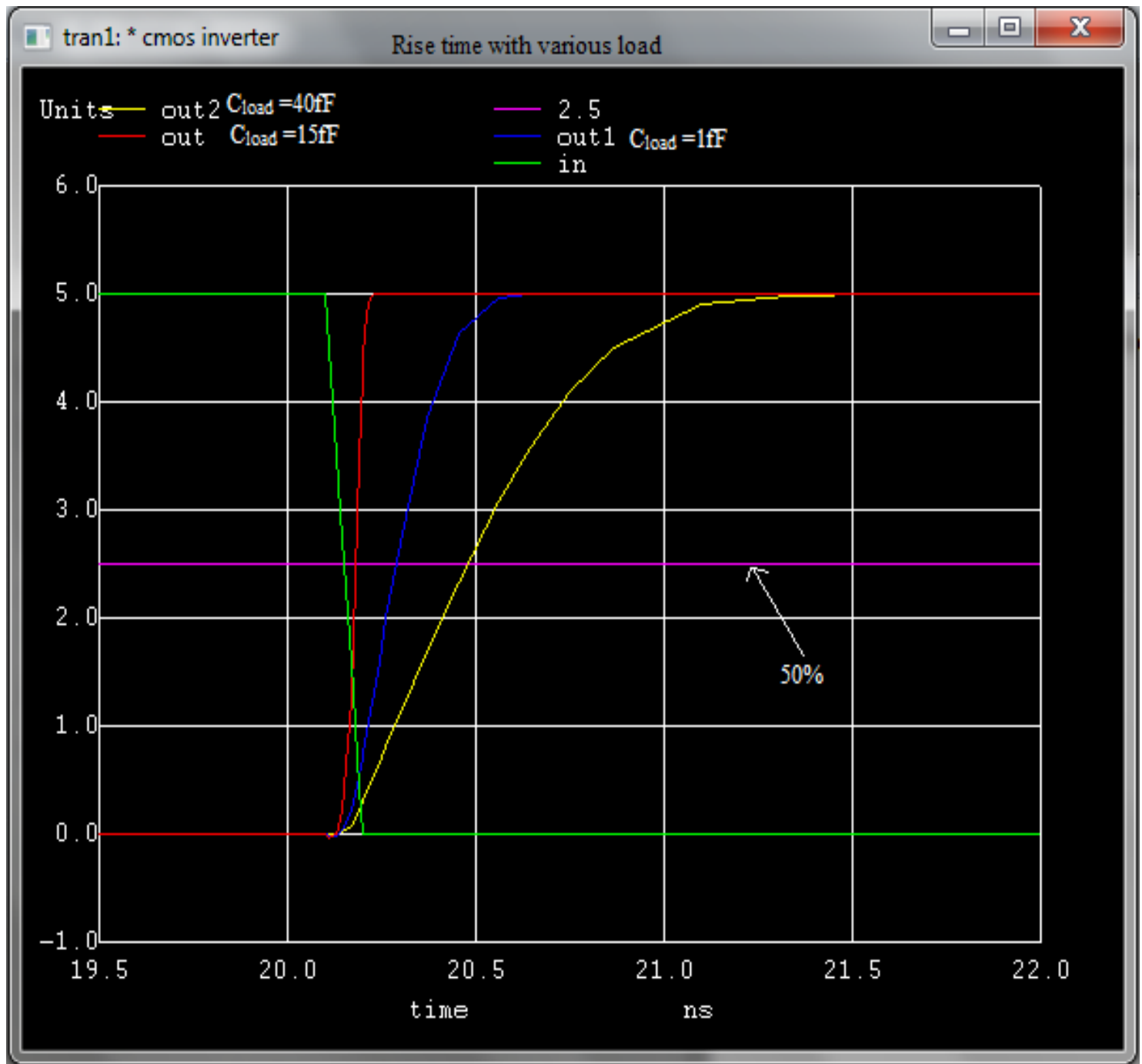


Nand :

 


Nand dc

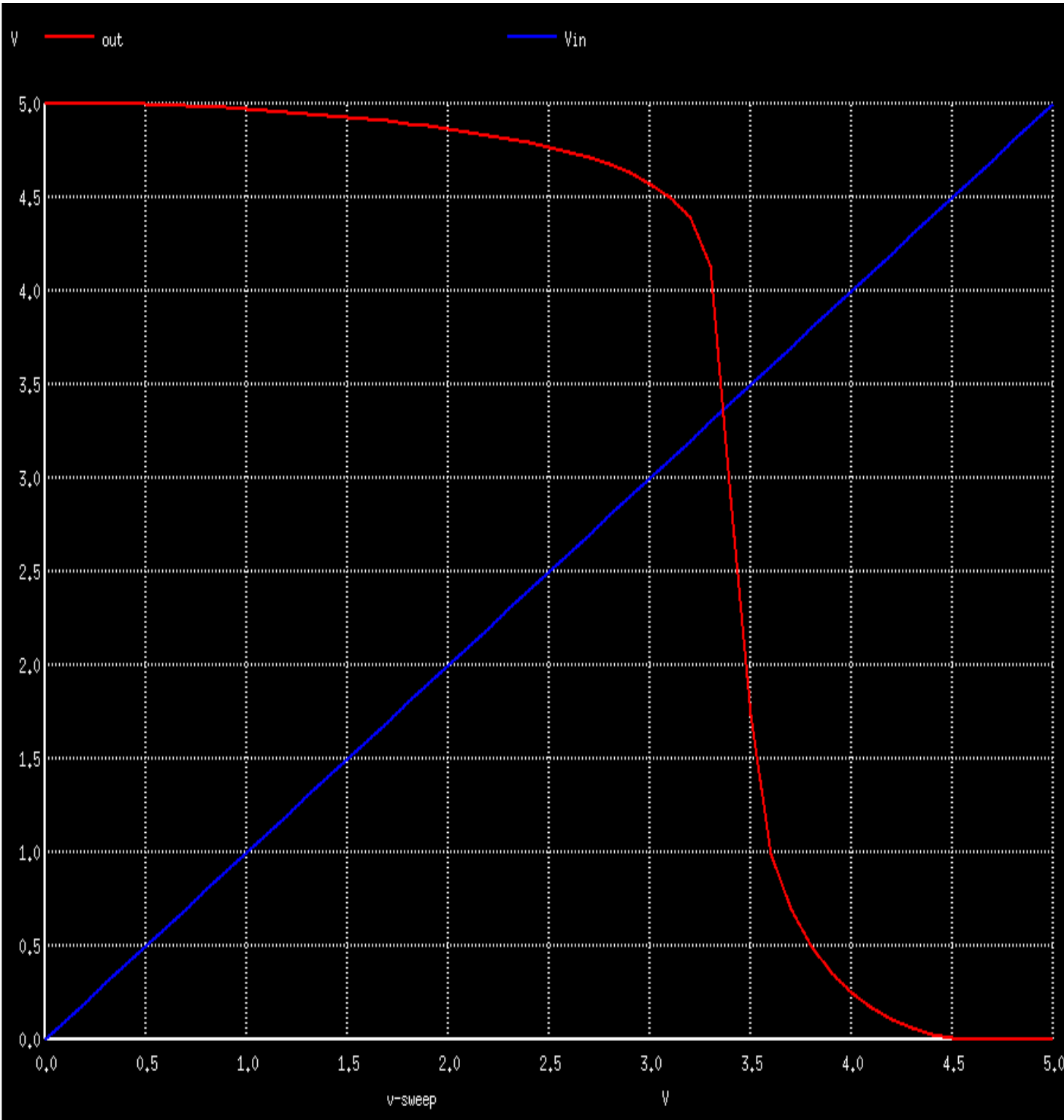


# Nor

 


Xor:

 

Nand Vsb effect

 


Aoi hazard

 




Aoi out

 

Aoi\_pseudo:

 

Aoi pulldown

